

555 Timer Sound Synthesizer

Bharat Raj-CB.EN.U4ECE22211

R P Nitheeshh-CB.EN.U4ECE22231

J Rosario Louie Jean-CB.EN.U4ECE22243

Siddarth Saravanan-CB.EN.U4ECE22252

B.Tech – ECE / CCE

Department of Electronics and Communication Engineering

Amrita School of Engineering, Coimbatore

19CCE384 Design and Innovation Lab

Exhibition Date:28/03/25

22ECC11


PROBLEM STATEMENT

Design a 555 timer-based sound synthesizer capable of generating 22 distinct tones. The circuit should provide stable frequency outputs. It should be able to drive a small speaker and maintain consistent sound quality. The design should be simple, cost-effective, and suitable for basic musical applications.




APPROACH / DESIGN/ METHODOLOGY

The 555 timer is set in astable mode to continuously oscillate and generate a square wave signal. 22 resistors are used to set different resistance values, allowing the circuit to produce 22 distinct tones. The square wave output from pin 3 of the 555 timer is fed to an 8Ω speaker, producing audible tones.


CIRCUIT DIAGRAM /ALGORITHM

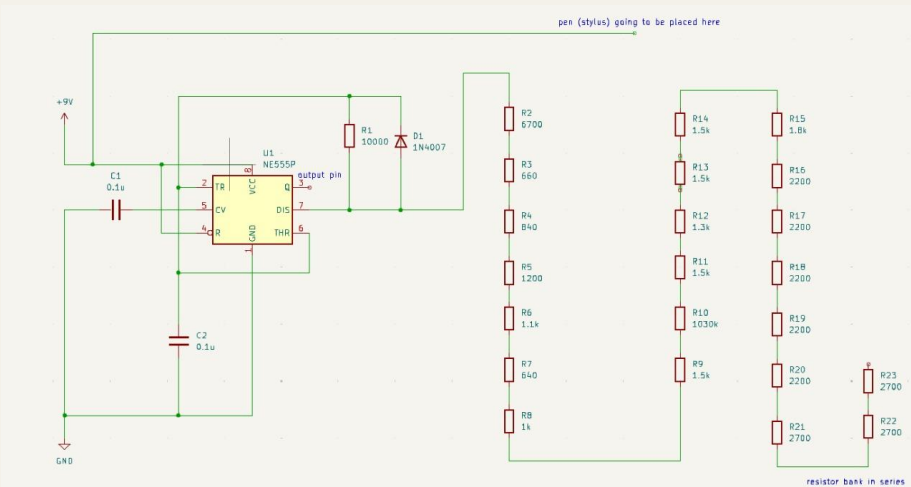


SIMULATION RESULTS

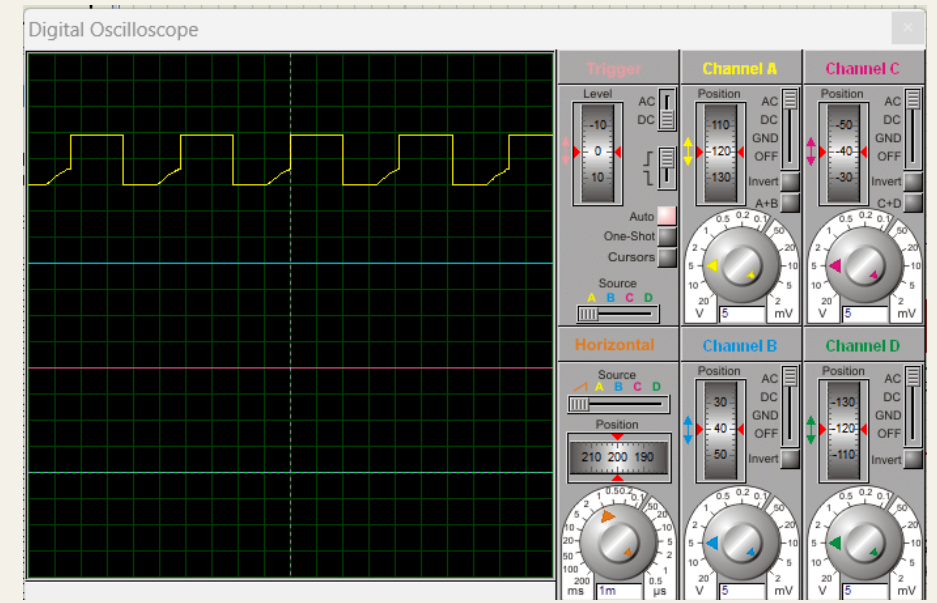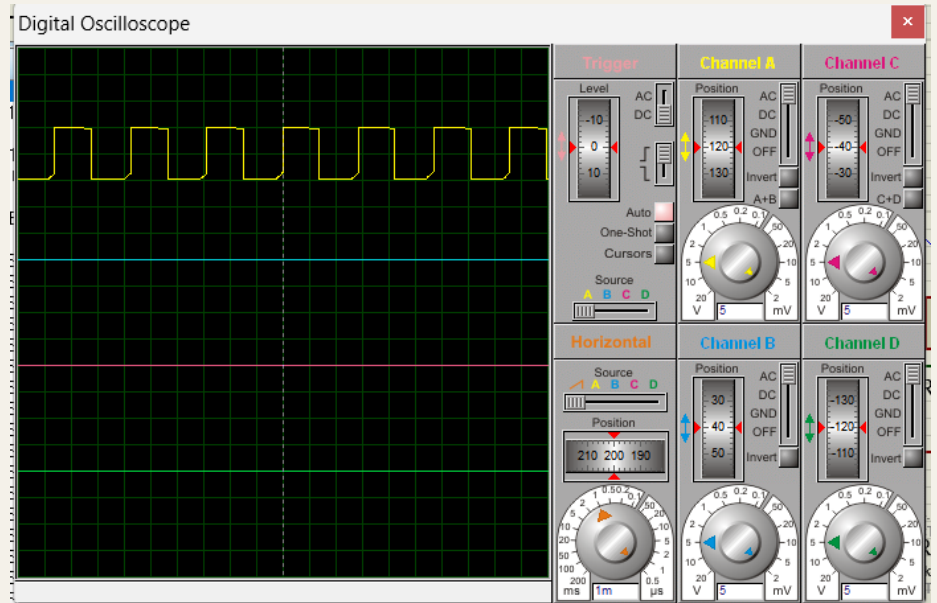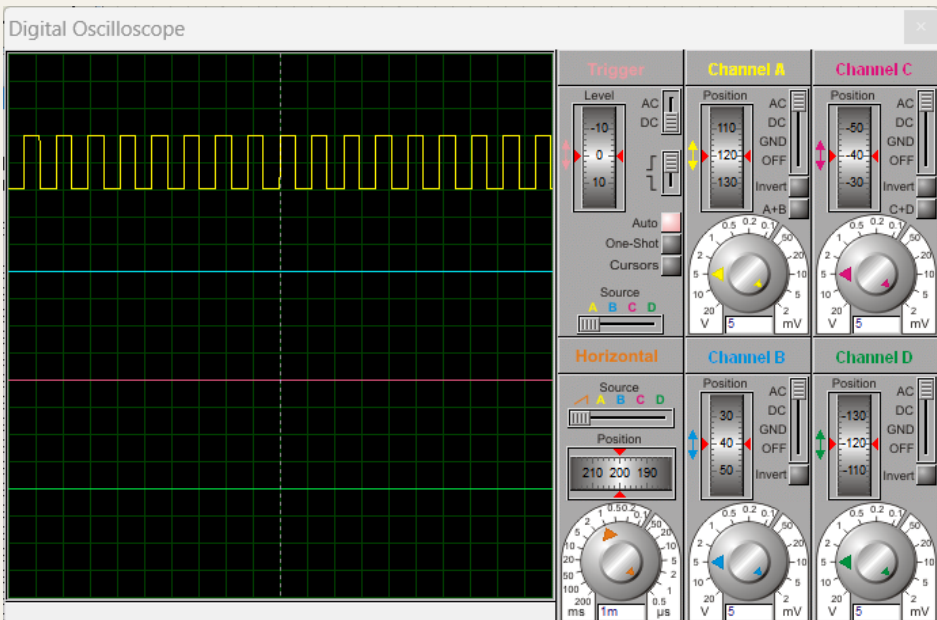


WORKING MODEL PICTURES

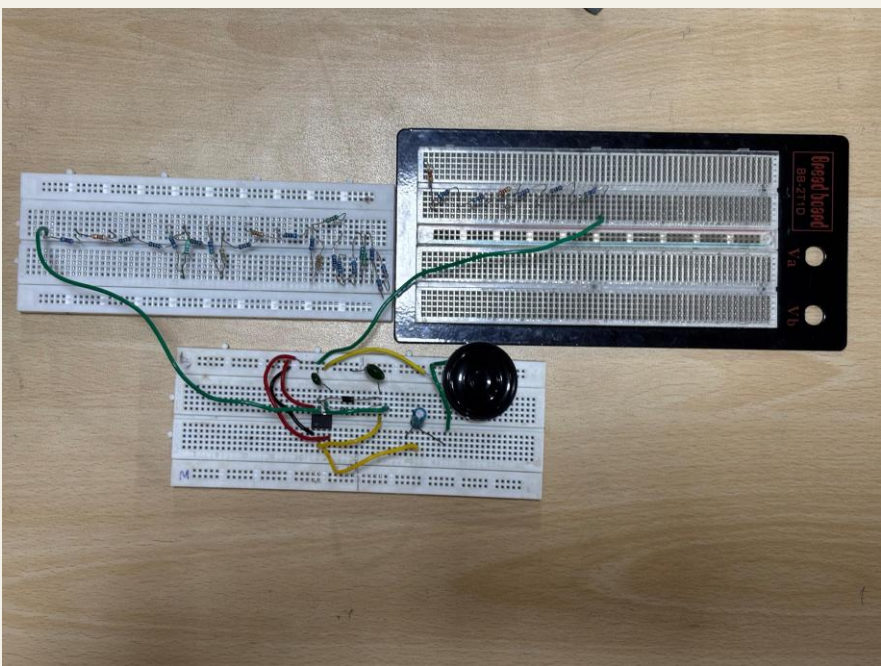

RESULTS/ CALIBRATION/ ERROR GRAPH

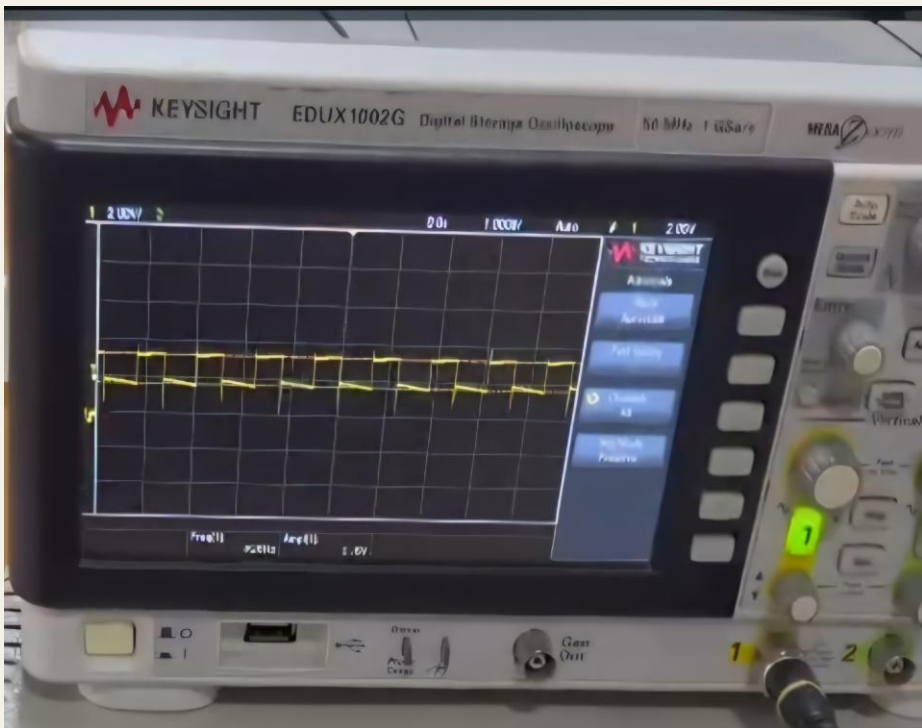

PCB LAYOUT

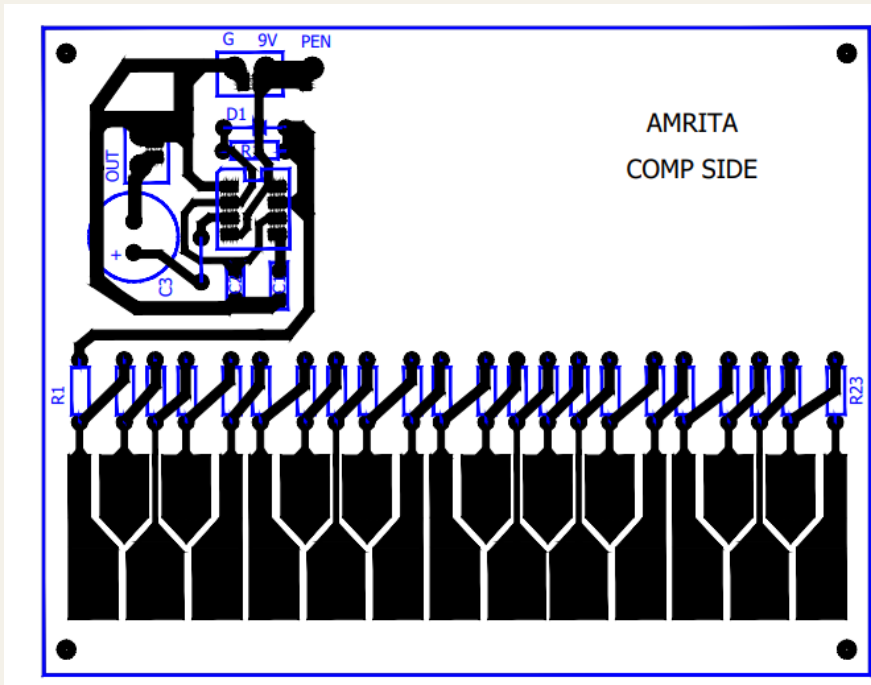

REFERENCES

- [1] A. Sedra and K. Smith, *Microelectronic Circuits*. S.L.: Oxford Univ Press Us, 2019.
- [2] Kristijan Nelkovski, "Create Your Own Stylus-Controlled Synthesizer," *Allaboutcircuits.com*, Dec. 08, 2024. <https://www.allaboutcircuits.com/projects/create-your-own-stylus-controlled-synthesizer/> (accessed Mar. 27, 2025).
- [3] drj113, "A Stylophone," *Instructables*. <https://www.instructables.com/A-Stylophone/>